

Name Waleed Akram

Roll 20P-0640

Manual # 09

Experiment performed.

Multiplexers

Types of multiplexers

De-multiplexers

Types of De-multiplexer

Applications of multiplexers &

De-multiplexers

Objective

The objective of this lab is to understand how to make different multiplexer and Demultiplexer can be obtained and used by using different logic gates by IC's



Used equipments

Wires

Bread Board

Digital experimental board

logic gates

Battery

Used software

Multisim


logic.ly

Multiplexer

Multiplexer is a device that has multiple inputs. E.g. ~~outputs~~ single line output

Multiplexer is also called as

Mux

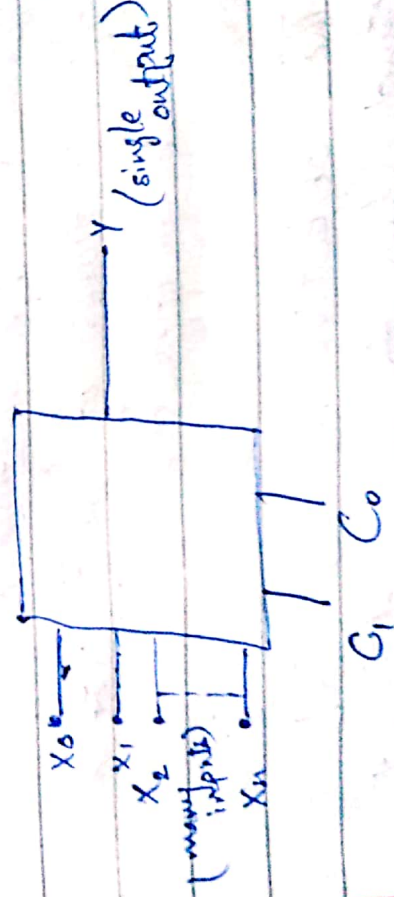

Types


4x1 Mux

8x1 Mux

16x1 Mux
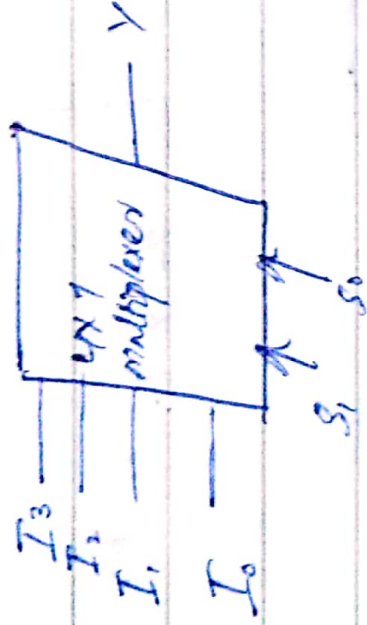
# 4x1 Mux


4x1 multiplexer has four inputs  $I_0, I_1, I_2, I_3$ . Two selection lines  $S_1$  &  $S_0$  and one output  $Y$ .



Truth table

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


4x1 Mux Diagram

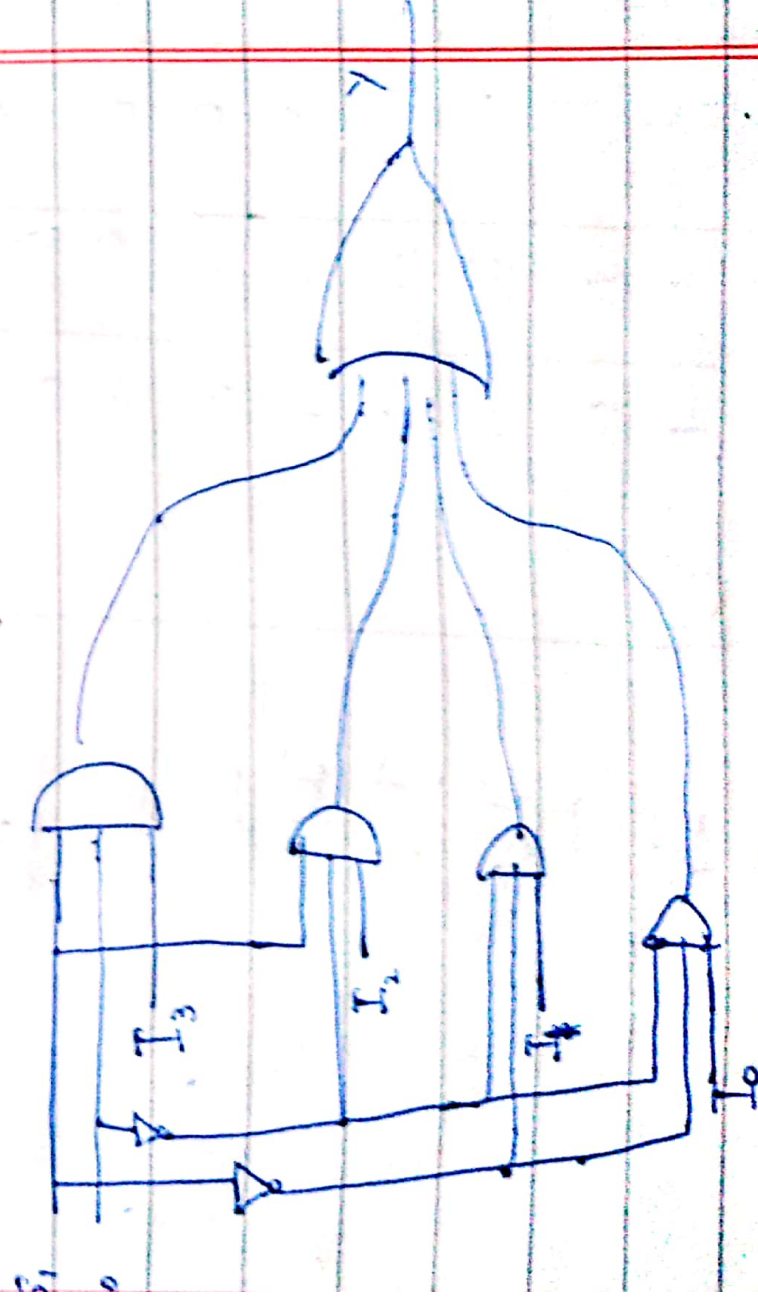


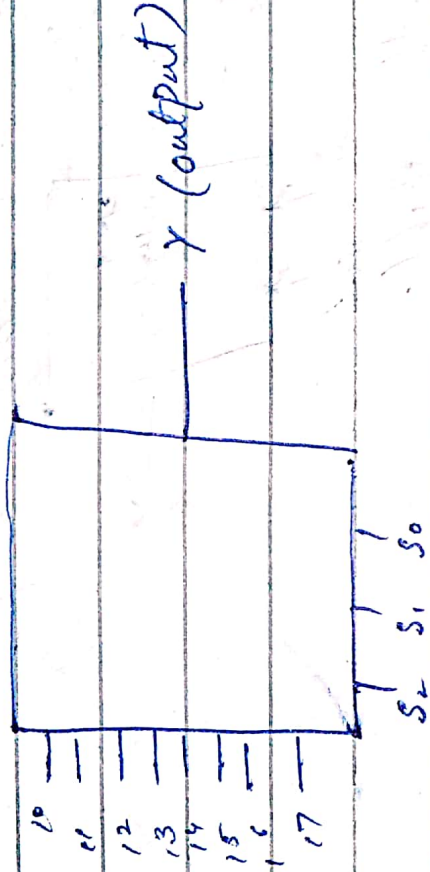
## 8x1 multiplexer

It has 8 inputs and 1 output having three selection lines  $S_2, S_1, S_0$



Expression


$$Y = S_2'S_1'S_0'I_0 + S_2'S_1'S_0I_1 + S_2'S_1S_0'I_2 + S_2'S_1S_0I_3 + S_2S_1'S_0'I_4 + S_2S_1'S_0I_5 + S_2S_1S_0'I_6 + S_2S_1S_0I_7$$

Truth table


input			output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

Date: / /

MUX

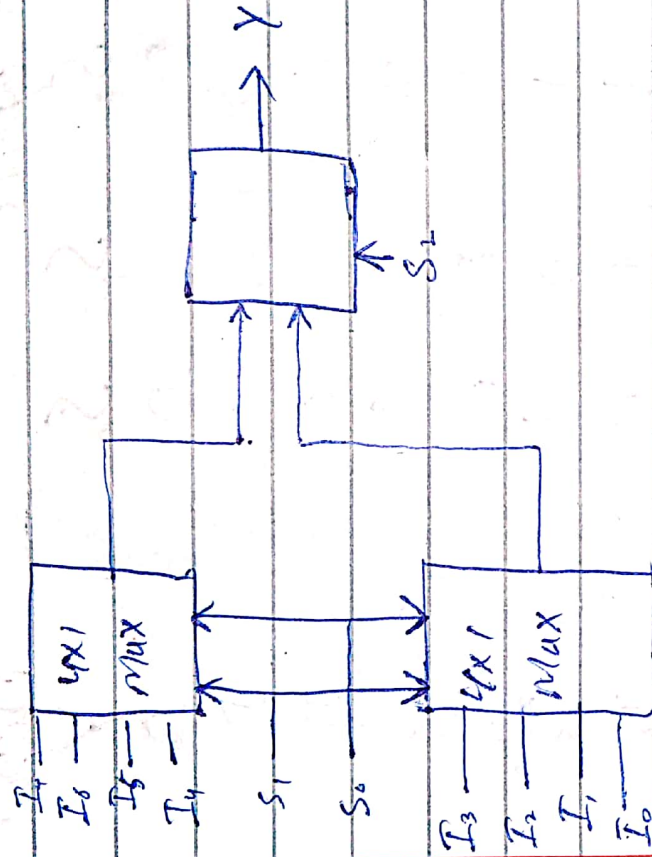

16x1 Mux

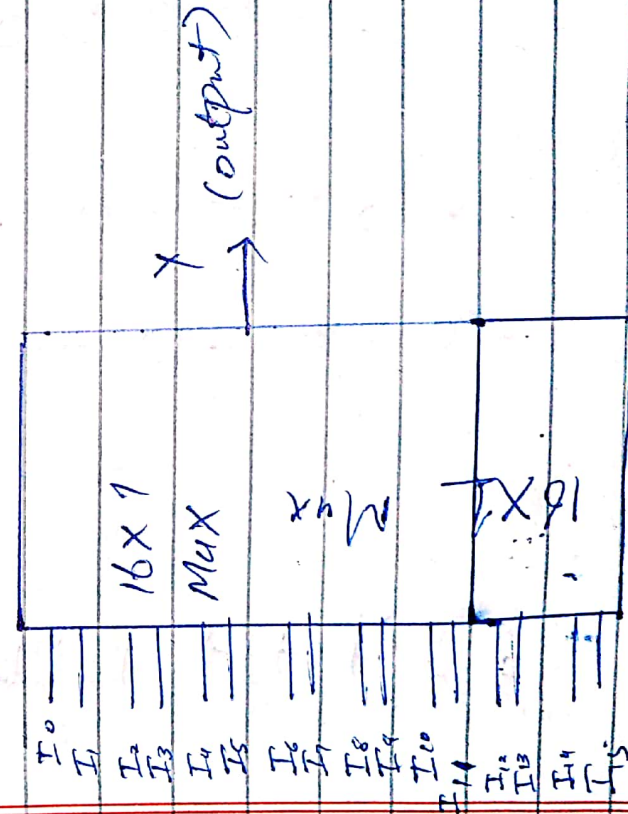



# Mux Truth Table


Output

Selection inputs

$S_3$   $S_2$   $S_1$   $S_0$


0	0	0	0	$I_0$
0	0	0	1	$I_1$
0	0	1	0	$I_2$
0	0	1	1	$I_3$
0	1	0	0	$I_4$
0	1	0	1	$I_5$
0	1	1	0	$I_6$
0	1	1	1	$I_7$
1	0	0	0	$I_8$
1	0	0	1	$I_9$
1	0	1	0	$I_{10}$
1	0	1	1	$I_{11}$
1	1	0	0	$I_{12}$
1	1	0	1	$I_{13}$
1	1	1	0	$I_{14}$
1	1	1	1	$I_{15}$

# 16 x 1 Mux

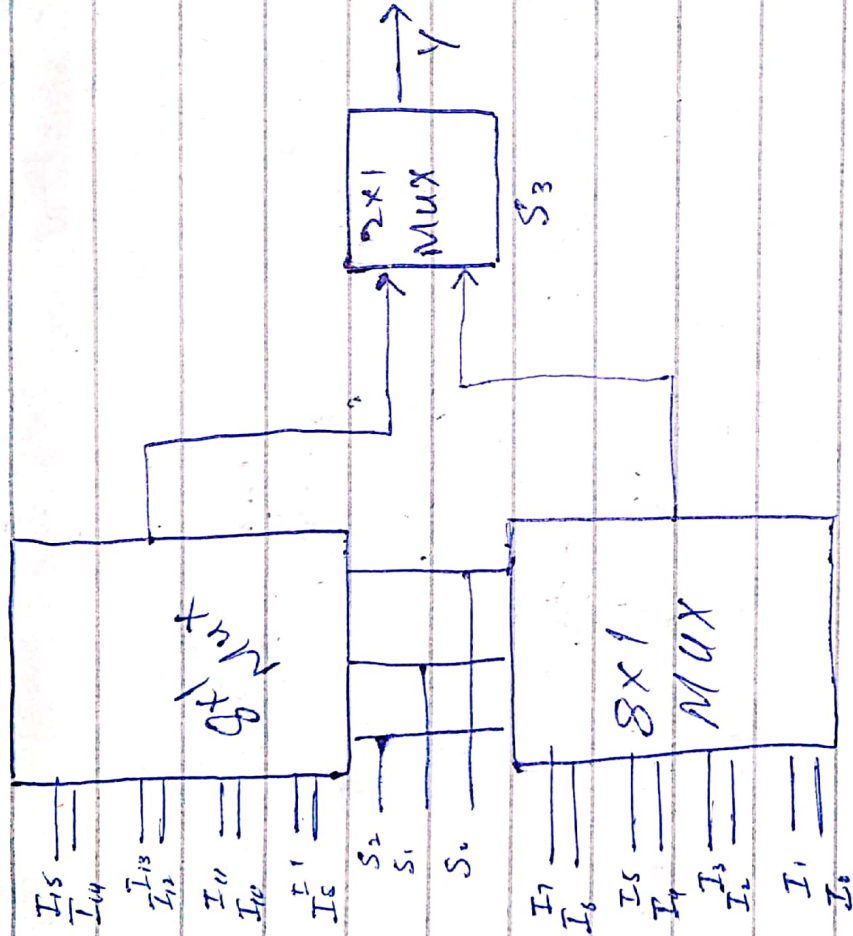
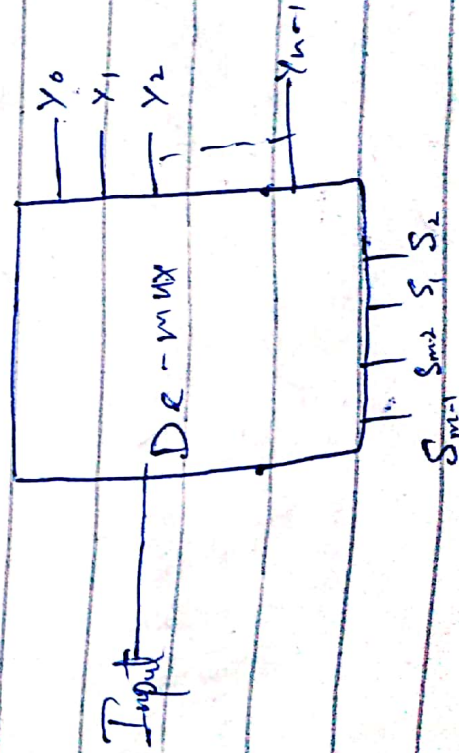
## Demultiplexer


Function of De-multiplexer is in contrast to multiplexer. It takes information from one line & distributes it to a given number of output line. It is also called Data Distributor.




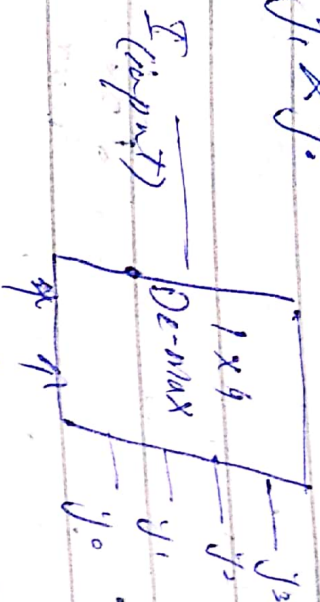
## 1x4 De-Mux

1x4 De-mux has one input I, two selection lines.  $S_1, S_0$  and four output lines.  $Y_3, Y_2, Y_1, Y_0$ .



Selection Input		output			
$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

## 2x4 De-Mux Diagram

$Y_3 = S_1 S_0 I$
$Y_2 = S_1 S_0 I$
$Y_1 = S_1 S_0 I$
$Y_0 = S_1 S_0 I$

## Conclusion

After studying about Max & De-Mux we are able to design them and use them into determine devices.