

Name **Malak Akram**
Roll no **20P-0640**

Lab Manual # **5**

Objective:


In this lab we study about ~~adders~~, Half adder, full adder and how to make a full adder from a half adder.

Adder:

Adder is conditional circuit which add binary numbers

Half adder:

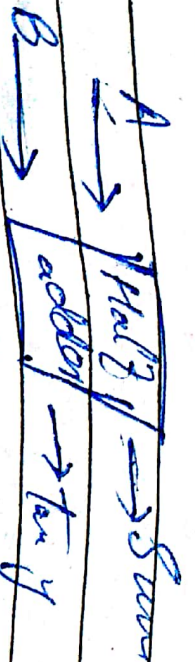In half adder we use input two binary two digits and output two binary digit in the form sum bit



Date: ___/___/___

Day: **MTWTFSS**

Truth Table


Input		Output	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = A \oplus B \Rightarrow A'B + A \cdot B'$$

$$\text{carry} = A \cdot B$$

Full adder

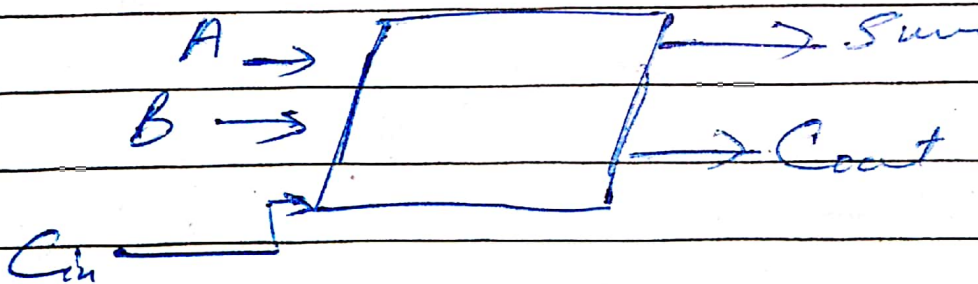It accepts two input and one carry input and produce a sum output and an output carry.



$$\text{Sum} = A \oplus B \oplus C$$

$$\text{Carry} = A \cdot B + (A \oplus B) \cdot C_{in}$$

Date: / /

Day: **M T W T F S**

Conclusion:

In this lab we learned what is half adder & about full adder & how to make full adder by adding two half adder