

Date: / /

06

Mon Tue Wed Thu Fri Sat

Name Waleed Akram

Roll no 20P-0640

Lab Manual 6th

* Experiment:

- full subtractor
- half subtractor

* Objective

How to make a subtractor
using different logic gates IC's.

* Equipments required for experiment:

- * Electricity / Battery
- * Wires
- * Bread Board
- * Logic gates
- * Digital experiment board.

* Software for simulation:

Multisim

Logicly

* Back Ground:

It is an electric circuit

which provides difference b/w two binary numbers & provides borrow as output

* Subtractor types:

Full Subtractor

Half Subtractor

* Half Subtractor:


Half subtractor produces difference b/w two binary bits at the inputs and also produces an output (borrow) to indicate if a 1 has been borrowed

Minued A $\xrightarrow{\text{Half Subtractor}}$ Difference (D)
Subtracted B $\xrightarrow{\text{Borrow}}$

A	B	D	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

#06

K-Map for difference (D):

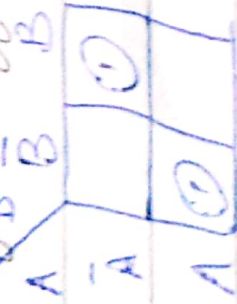


$$D = A \oplus B$$

K-Map for Boolean



$$\text{Boolean} = \bar{A} \cdot B$$

Circuit Diagram

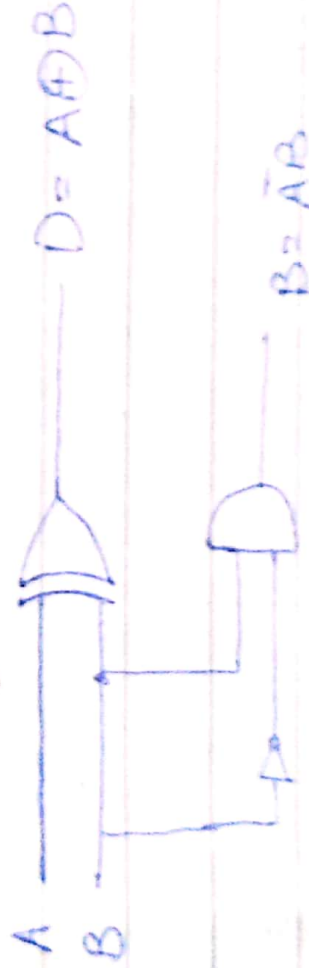

K-Map (Full subtraction)

A \ B(in)	B(in)			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

The equations for the difference as well as B(out) are mentioned


below

A \ B(in)	B(in)			
	00	01	11	10
0	0	1	1	1
1	0	0	1	0

$$D = A'B'Bin + AB'Bin + A'BBin$$

+ ABBin for borrow expression

$$B(out) = A'Bin + A'B + BBin$$

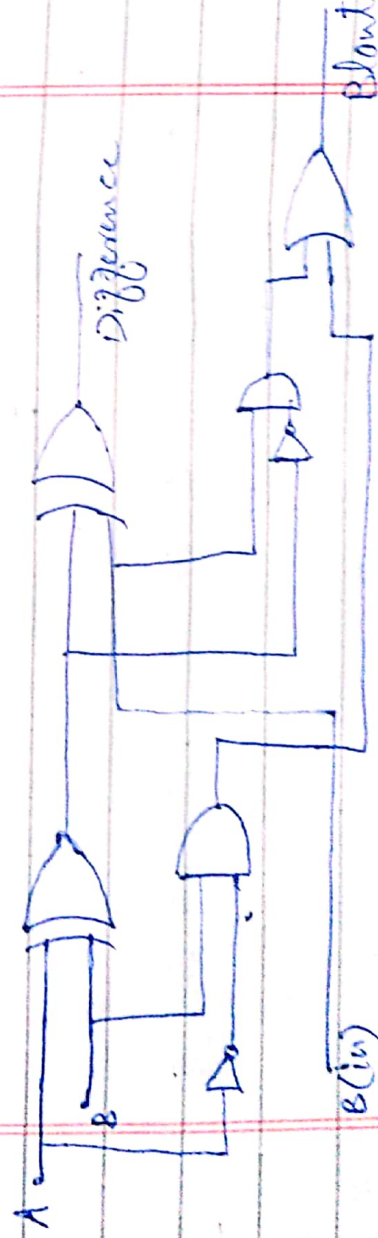


Conclusion

After performing above experiment we understood the designing and processing of Half and full subtractors. And its application and uses in circuits

06

Full subtractor

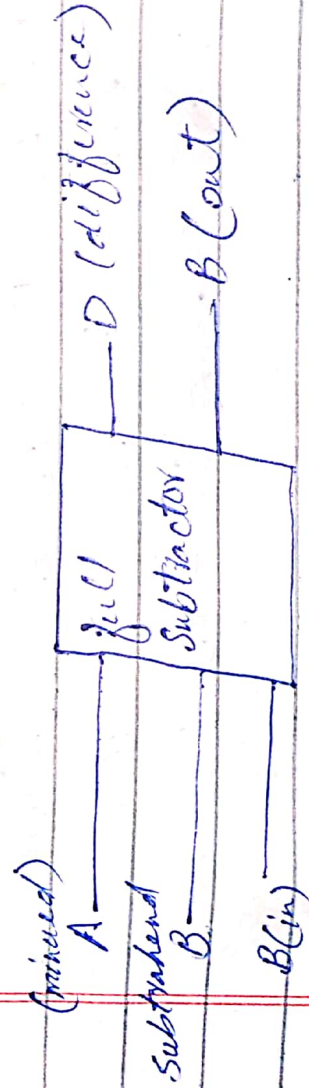A full subtractor is a combination circuit that performs subtraction of two bits, one is minued & other is subtrahend, taking two into account borrow of previous adjacent lower minued bit. This circuit has three inputs and two outputs.



A	B	B(in)	D	B(out)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1